

"THE SWEEPER"

A unique method of determining SWR.

W9BTI June 1954

How many times have you VHF men wished that you had a SWR indicating device that would take over where most other SWR meters start to drop off and get inaccurate as the frequency is raised? The meter about to be described is just such a device. Its effectiveness first starts at about 50 MC and gets better as the frequency rises. The SWR indicator described here was designed for the 2 meter band, but by increasing or decreasing the length of the tuned lines it can be adapted for "your band" be it 50, 144, 220, or 420 MC. It is essentially a SWR of the sweep oscillator and oscilloscope type. It has been suggested in literature* and is used by TV stations cable manufacturers etc. I have not to this date seen it described in any amateur publication so therefore I am passing it along to all those interested. Those that have used them praise them for their accuracy, simplicity of connection, ease of reading results and the ability to see directly the results of your adjustments of your antenna matching device. Since the device is basically a swept oscillator, it will be referred to from now on as "The Sweeper".

Before construction and application details are given, it might be wise to consider the theory of the sweepers operation. Consider the operation of a transmission line. When one end is terminated with a resistor that is non-reactive and is equal to the lines surge impedance then the impedance seen at the other end will equal the surge impedance. This holds true for any radio frequency fed into the line. If the far end of the line is left open instead of having it terminated as above, then the impedance seen at the other end will depend on the length of the line and the frequency of the signal fed into it. As an example, a frequency which would make the unterminated line an even number of quarter wave lengths long would cause the impedance at the sending end to be very high. If this same unterminated line was fed a frequency that made the line an odd

~~number of quarter wave lengths long the impedance at the sending end would be very low.~~

WSBY, JUNE 1954

impedance seen at the sending end would be zero. If the same lines far and were shorted, then the results of the two examples above would be just the opposite, that is, in the first case the sending end would see a short and the second case it would see an infinitely high impedance. Frequencies occurring between these two extremes would cause the sending end to see a impedance varying from dead short to infinitely high. When the sweeper is attached to a line, and it sweeps over a range of frequencies, the impedance it sees will depend on what is connected to the other end of the line. If the line is terminated in the lines surge impedance the the sweeper sees a steady impedance equal to the surge impedance of the line, and will reproduce a straight line trace on the scope. But if the line is improperly terminated (a mismatch) then the impedance seen by the sweeper will vary with each frequency in the swept range. Since the frequency in the sweeper is being swept at a 60 cycle rate, the the impedance will vary at a 60 cycle rate. This changing impedance with its consequent varying voltage across it, is detected in the sweeper by a crystal diode. This voltage is 60 cycle AC with an RF component. After the RF is filtered out it is fed to the vertical amplifier of a scope. The scopes time base is also 60 cycles and is in phase with the sweeper so a sine wave trace appears on the screen. The amplitude of the sine wave indicates the degree of mismatch. So the object of your antenna adjustments is to reduce the sine wave amplitude to a straight line. I might add at this point that a fairly straight line can be easily obtained on a transmission line that is terminated in a carbon resistor of proper value and whose lead length is zero. However when the line is terminated in an antenna the task of getting a straight line is more difficult. There is a reason for not getting a pure straight line when it was terminated in a proper resistor in that there is no such thing as a perfect cable available commercially; but now with the antenna attached the load is frequency sensitive. You will note on the scope that

certain antennas can be made to produce a straight line over almost the entire screen whereas some are only flat for about one third of the screen. See diagram 1^{J61}. This indicates the bandwidth of your antenna. Broadside arrays with few parasitic dipoles are quite flat and can be matched over the entire four MC sweep. However most high gain yagi's are very narrow in band width and show it on the scope. This fact must be borne in mind when using the sweeper so that you don't try to get some result that is theoretically impossible due to the type of antenna being adjusted. Let us say that the sweeper is attached properly to a 100 foot piece of RG8U, 52 ohm cable, and that the cable is properly terminated with a 52 ohm load, be it a resistor or antenna. The pattern on the scope will be a straight line as in the group of patterns of Fig 1 A. If the cables load is disconnected and left unterminated, the pattern at 1 B will result. If the cables load end is shorted then the same pattern will result but will have a 180 degree phase difference as in 1 C. If the 52 ohm cable is terminated, let us say with a 500 ohm resistor, a pattern as in 1 B will result. As the value of the resistor is reduced the sine wave pattern will gradually reduce in amplitude as in 1 D, which happens to be 100 ohms or a SWR of 2 to 1. As the resistor is brought near the cables surge impedance (52 ohms), the sine waves amplitude will reduce to zero and result in a straight line, as in 1 A. This is a SWR of 1 to 1. The number of sine waves that appear on the scope depends directly on the cable length. If the cable is too short, ie, if less than one half of a sine wave appears, then it would be advisable to add cable just for the test and remove the piece after you have made your antenna adjustments and have reduced your SWR. 100 feet is a very satisfactory length for 2 meters.

The frequency of a 955 oscillator tube is varied or swept across the band desired. The sweeper described is set up for the 2 meter band, so from now on dimensions referred to will be for the 2 meter band.

The sweep width can be set on a panel control from zero to 8 MC. The 2 meter band is 4MC wide so that will be all the sweep needed.

However you may want to see how your SWR is out of the band so that is why 8 MC sweep width was included. The sweep control is a rheostat that adjusts the amount of 60 cycles AC voltage fed to the sweeper motor, which is from a surplus ARN 1 altimeter receiver-transmitter. One quarter of a volt 60 cycles AC sweeps 4 MC.

Two circuits are included, the deluxe and the economy. Both do an excellent job and have equal accuracy. The deluxe circuit has a different scope presentation and enables you to check line losses, and is easier to interpret. The deluxe sweeper has a retrace blanking circuit built within. The circuit used actually stops the sweeping oscillator from oscillating when the sweep motor has reached its limit of excursion and is going to return and produce a retrace. The retrace is presented on the scope as a base line. The exact point where the oscillator is stopped and started is adjustable by means of the phase control included in the deluxe circuit. This adjustment is necessary to sync the action with the sweep motor and scope. The higher the line losses, the greater the distance between the base line and the negative excursion of the trace. If the line has zero loss (impossible), then the negative excursion will coincide with the base line. A phasing control and an oscillator blanking switch is incorporated in the deluxe model to adjust for a correct scope pattern. On the economy circuit the pattern can be made clearer if the scope is equipped with retrace blanking and a phasing control.

The sweeper is equipped with a rough and a fine frequency control. The rough control is set so that the fine control adjusts the operating frequency only within the 2 meter band.

The output of the sweeper is terminated in two coaxial panel receptacles. It is wise to make one the popular SO239, and the other a UG-58/U so as to make the instrument more versatile. On coax checking, attach the cable to the receptacle that fits its connector and cover the other unused fitting with a coax cover which has been modified to short the receptacle to ground with a low inductance path. Two covers will be necessary, each one with it

special shorting plug soldered within it. For 300 ohm line checking, both covers are removed and a wire from each side of the 300 ohm line is connected to each coax receptacle.



The sweeper has its own power supply within it and is isolated from ground. A 117 volt receptacle is also included so as to have a place to plug in the scope. The scope need not be an elaborate one and need not have a high frequency response. 60 cycles is the highest frequency measured. The scope must have a sync system that can be coupled to the line for sync with the sweeper. 99% of scopes are so equipped.




The sweeper can be built in a box 3"by 5"by 10" or what have you. No attempt will be made here to indicate exact construction details. The basic oscillator dimensions and circuit values will be given. So build in what you have and how you like to. The places where special care and short leads are an absolute necessity will be indicated. In building the sweeper see the mounting diagrams and drill or punch holes to fit the parts you are going to use. This also depends on which model you are going to build. Short leads are definitely required in the assembly of the diode detectors, coax connectors, load resistors and the pickup line. The construction of this portion is referred to in Fig. 3.

After the assembly has been completed, testing and calibrating must be started. Set the variable capacitor to mid scale. Tune a 2 meter receiver to 146 MC. Turn sweep width control to zero. Tune the oscillator to 146MC by listening in the receiver and adjusting the shorting bar on the oscillator long lines. The dial is now centered in the 2 meter band and other points on the dial may be marked by listening for the oscillator in the calibrated receiver. From now on wherever you set the dial the sweeper will sweep on both sides of this spot. How far it sweeps depends on how far you advance the sweep width control. We usually leave it at center scale, or 4 MC sweep. After you start to use the sweeper and you have your antenna as flat as you think you can possibly get it, turn the sweep width control to zero and listen for the signal in a calibrated

2 meter receiver. The frequency that the signal is picked up at is the center of the bandwidth of your antenna. If it is not in the portion of the band that you use, you may want to readjust your matching device and possibly the length of your antenna elements to bring it on frequency. I have seen some antennas flat only outside the 2 meter band. It is obvious that more work on the antenna is necessary. To use the sweeper, attach the vertical amplifier of the scope through a shielded cable to the connection for it on the sweeper. Set the time base to line frequency and sync the scope to 60 cycles. Some scopes have a built in source of 60 cycles. Those that don't will have to couple the horizontal amplifier to about 6 volts 60 cycles as supplied by a small filament transformer. Set the sweep width to 4 MC. Set the frequency dial to 146 MC. Couple the antenna to be checked to the sweeper with at least 100 feet of cable to the coaxial receptacles desired. Be sure the shorting cover is on the unused receptacle. If 300 ohm line is used, take both covers off and connect one side of the 300 ohm line to each one. Be sure that the excess line is not coiled up, but is stretched out and away from all objects. It can be suspended on string during the test. Excess coax can be coiled up, but never ribbon or open line. Adjust the vertical gain of the scope so that the trace occupies about $2/3$ of the screen height. If the vertical size of the trace is not great enough, your scope lacks vertical sensitivity. This can be corrected without too much inaccuracy, by completely removing R5, the oscillator output terminating resistor, or substituting a more sensitive scope. Advance the horizontal gain so that the trace occupies about 80% of the screen width. Refer to the diagrams of patterns obtainable and check your particular condition. You can determine if its scope adjusting, sweeper controls or antenna that has to be adjusted for correct patterns. After the scope controls, height, phasing, blanking etc, and the sweeper controls are set ok then proceed with antenna adjustments. Adjust for a trace that indicates a SWR of 1 to 1 or as close as you can come to it.

PATTERNS INVOLVING 100' RGSU WITH VARIOUS TERMINATIONS SAME FOR ALL CABLES	DE LUXE SWEEPER PHASING CORRECT OSCILLATOR BLANKING ON	DE LUXE SWEEPER PHASING CORRECT OSCILLATOR BLANKING OFF	DE LUXE SWEEPER PHASING INCORRECT OSCILLATOR BLANKING ON	ECONOMY SWEEPER SCOPE PHASING CORRECT	ECONOMY SWEEPER SCOPE PHASING INCORRECT	ECONOMY SWEEPER SCOPE PHASING INCORRECT BUT SCOPE HAS BEAM BLANKING ON	DE LUXE SWEEPER OK ORG. DIAL WITH SBT ATTCH
FIGURE 1	SWEEP 4MC	SWEEP 4MC	SWEEP 4MC	SWEEP 4MC	SWEEP 4MC	SWEEP 4MC	SWEEP 4MC
LINE A TERMINATED IN ITS SURGE Z (52Ω)							
SWR 3 TO 1							
LINE B UNTERMINATED							
FAR END OF LINE SHORTED							
52Ω D LINE TERMINATED WITH 800Ω							
SWR 6 TO 1							
52Ω E LINE TERMINATED WITH 100Ω							
SWR 20 TO 1							
52Ω F LINE TERMINATED WITH 75Ω							
SWR 1.5 TO 2							
CABLE G PINCHED AND NOT TERMINATED							
LOOSE JOINTS AND END SHORTED NOTE GRASS							
LINE I ATTACHED TO BROAD BAND ANTENNA							
LINE J ATTACHED TO NARROW BAND ANTENNA							

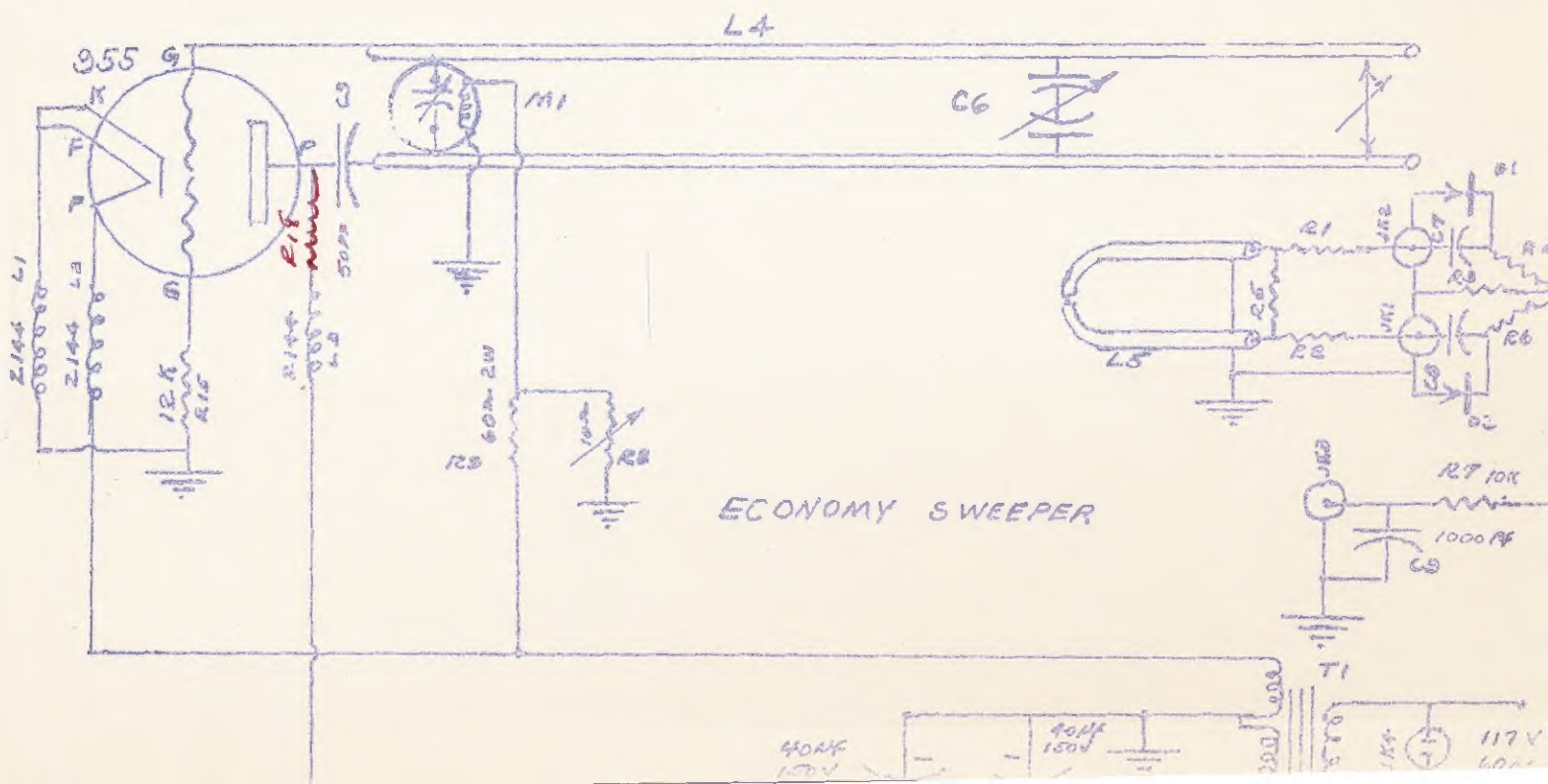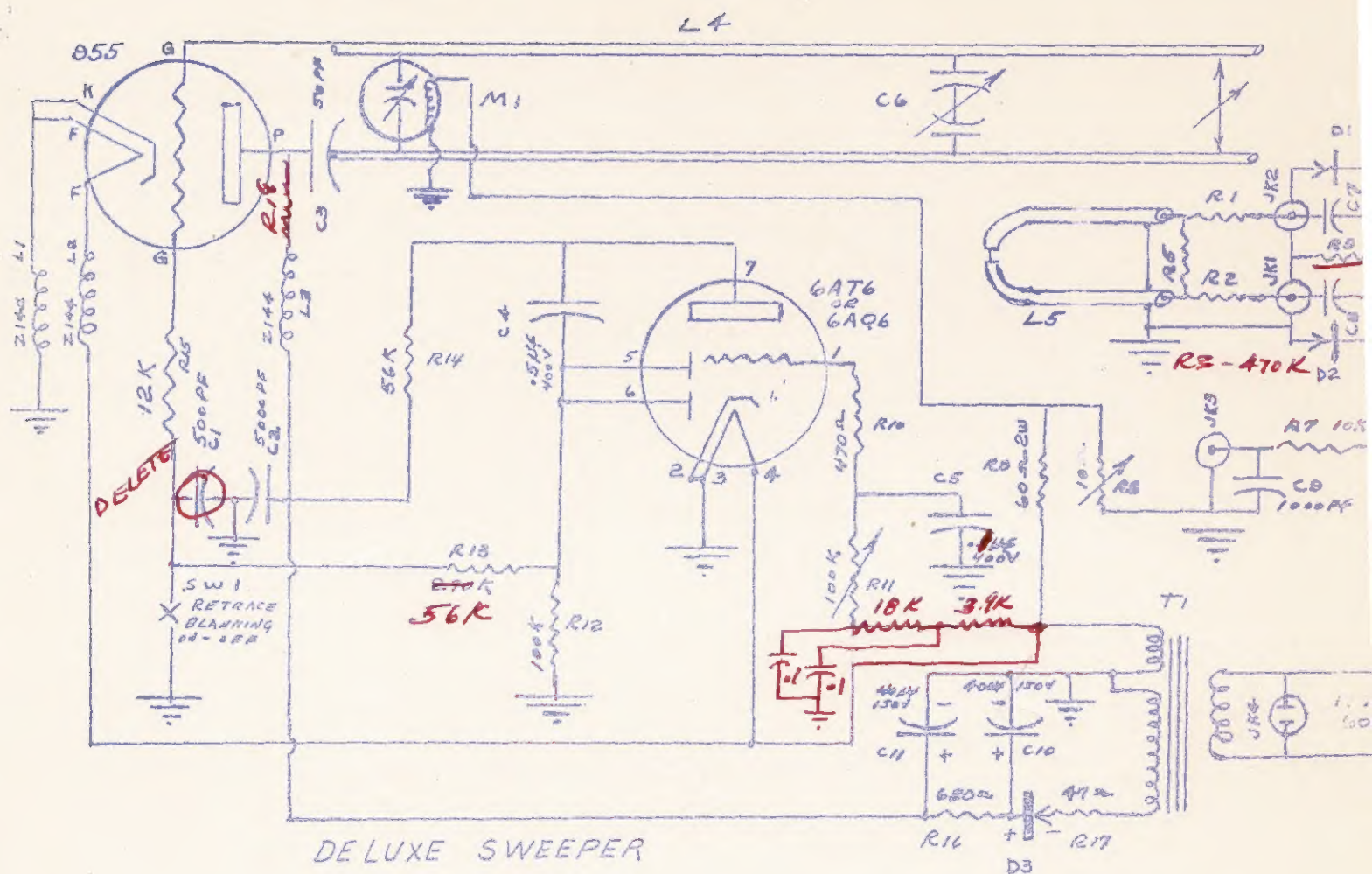

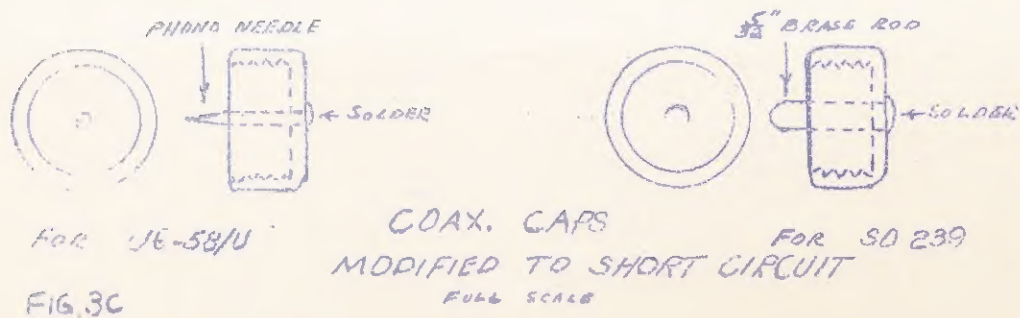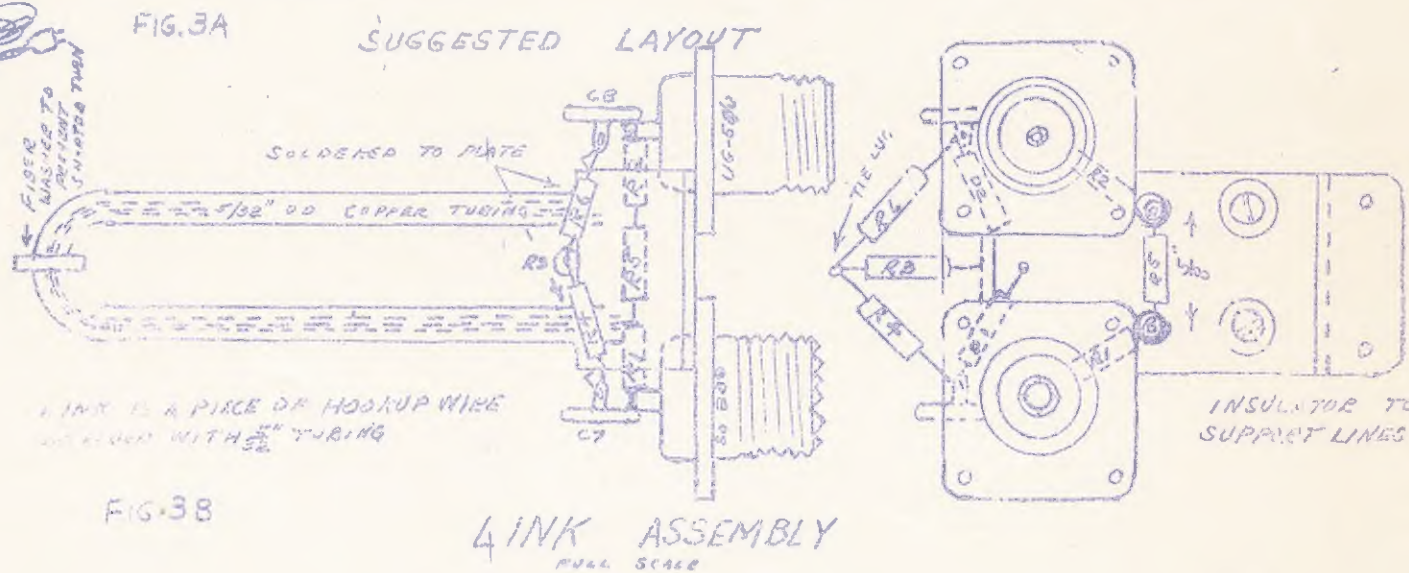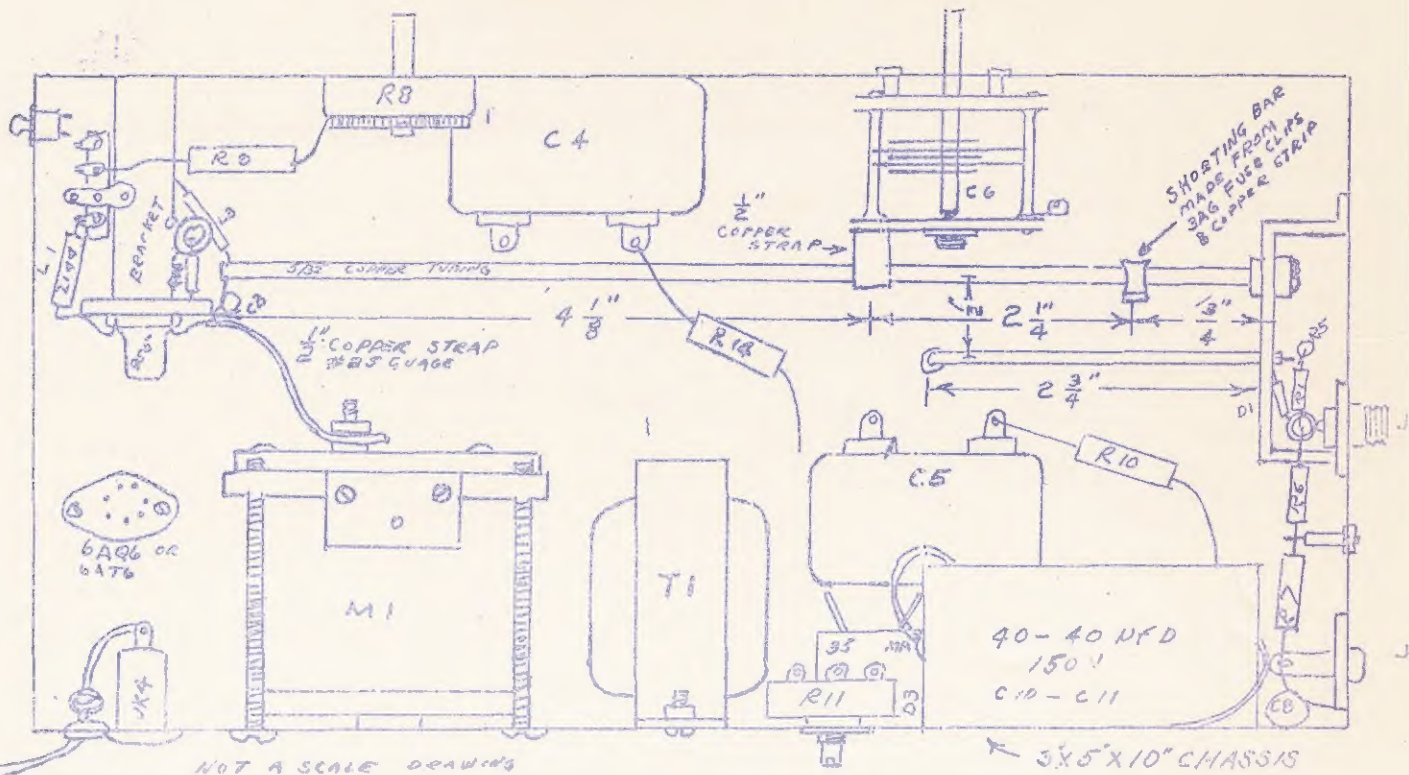

Other uses for the "Sweeper".

Checking the input impedance of receivers.

Checking the output impedance of noise generators.

Finding the impedance of unmarked cables.

Determine if the cable has a kink or some other discontinuity.

Transmission line which has a flaw, such as a pinch or partly open outer shield will cause a discontinuity to appear on the scope pattern as shown in Fig 1 E.

Aids in search for correct values of dummy loads for testing transmitters.

Location of noisy connections in transmission lines.

Noisy connections will show up as grass on the otherwise smooth standing wave trace and its base line.

PARTS LIST

R1, R2, R5, 100 ohm 1/2 W 5% Carbon	C1, 500 PF	Ceramic Capacitor
R3, 100K 470K " " "10%"	C2, 5000 PF	" "
R4, R6, R7, 10K " " " " "	C3, 50 PF Silver Mica Button	" "
R8, 10 ohm WW Rheostat 5W	C4, 0.5 0.5 MFD. 400V Paper	" "
R9, 60 " 2W WW or Carbon	C6, Butterfly 5 plate from SCR522	" "
R10, 470 " 1/2W 10% Carbon	C7, C8, 500PF Silv. Mica Button	" "
R11, 100K Potentiometer	C9, 1000 PF Ceramic	" "
R12, 100K ohm 1/2W 10% Carbon	C10, C11, 40-40 MFD 150V Elect.	" "
R13, 270K 5K 1/2W " "	D1, D2, 1N64 or CK710 Diode	" "
R14, 50K " 1/2W " "	D3, 35MA Selenium Rectifier	" "
R15, 12K " 1/2W " "	JK1 SO239 Coax Panel Receptacle	" "
R16, 680 " 2W " "	JK2 UG-58/U " " "	" "
R17, 47 " 1/2W " "	JK3 Phone Jack-CHinch	" "
L1, L2, L3, Z144 RF Choke	M1 Sweep Capacitor-Motor assy. from APN	" "
L4, L5, See Diagram	T1 Power Trans. 6.3V, 1Amp. 100V, 35MA	" "

R18 6.8K 1/2W

C5 3X.1 MFD 400V
117V Pri. as used in TV boosters etc.

The necessity of zero lead lengths on load resistors and the coax lead to them is made evident by this test.

* Sams PF INDEX #36 Jan 1953 P93

Radio News Sept. 1949 P52

